

---

## Chapter 15

# Formal verification of NCL circuits

*Ashiq Sakib<sup>1</sup>, Son Le<sup>1</sup>, Scott C. Smith<sup>1</sup> and  
Sudarshan Srinivasan<sup>1</sup>*

---

Validation is a critical component of any commercial design cycle. Testing-based approaches have been predominantly what has been used to ensure design correctness. Formal verification is an alternate approach to design validation, where correctness is established using mathematical proofs. Since a proof can correspond to a very large number of test cases, formal verification has been found to be extremely useful in establishing design correctness and finding corner-case errors that often escape traditional testing. Since the now infamous FDIV bug (i.e., bug found in the floating-point unit of the Intel Pentium processor in 1994 after shipping, which cost Intel \$500 million to correct), the semiconductor industry has aggressively incorporated formal verification into its design cycle for validation.

AQ1

AQ2

One of the more popular formal verification approaches that have been found to be extremely scalable and useful in semiconductor design is equivalence checking. Typically, a lot of time, money, and effort are invested into ensuring the correctness of a design. However, the design itself is never static, as it is continuously tinkered with and optimized. Equivalence checking technology can, with a high degree of automation and efficiency, check that the golden model (i.e., the design that has been extensively validated) and its derivate are functionally equivalent. Scalability is harnessed by exploiting the structural similarity of the golden model and its derivate. Examples of commercial equivalence checkers include IBM Sixth Sense, Jasper Gold Sequential Equivalence Checker, Calypto SLEC, Mishchenko EBCCS13, and Cadence Encounter Conformal Equivalence Checker.

In this chapter, we describe an equivalence checking methodology for NCL circuits. Note that currently, there are no commercial equivalence checkers for QDI circuits. For commercial applications, NCL circuits, and QDI circuits in general, are often synthesized from synchronous intellectual property designs. The resulting NCL design may then be further optimized and tinkered with. Therefore, we have designed an equivalence checker that can be used in two ways: (1) to verify the functional equivalence of two NCL designs and (2) to verify the equivalence between an NCL design and a synchronous design.

AQ3

<sup>1</sup>Department of Electrical and Computer Engineering, North Dakota State University

AQ4

## 15.1 Overview of approach

Vidura *et al.* [1] have previously developed an approach for verifying the equivalence of an NCL circuit against a synchronous circuit. They use the theory of Well-Founded Equivalence Bisimulation (WEB) refinement [2] as the notion of equivalence. In WEB refinement, both the circuit to be verified (here the NCL circuit) and the specification circuit (here the synchronous circuit) are modeled as transition systems (TSs), which capture the behavior of the circuit as a set of states and transitions between the states. WEB refinement essentially defines what it means for two TSs to be functionally equivalent. Their approach performs symbolic simulation on both the NCL circuit and the synchronous circuit to generate the TSs corresponding to both circuits. A decision procedure is then used to verify that the two TSs satisfy the WEB refinement property.

In working with the above approach, we found that because NCL circuits exhibit highly nondeterministic behaviors, the corresponding TSs are very complex, even for relatively simple circuits. This complexity leads to two issues. First is state space explosion. Second, it becomes very difficult to compute the reachable states of the resulting TS. Computing reachable states is important because unreachable states often flag numerous spurious counterexamples, which makes verification intractable.

We have therefore developed an alternate approach to circumvent having to deal with the NCL TS. The high-level idea is to perform structural transformation on the NCL circuit netlist to convert the NCL circuit into an equivalent synchronous circuit. The converted synchronous circuit is then compared against the specification synchronous circuit, using WEB refinement as the notion of correctness. The converted synchronous circuit, specification synchronous circuit, and the WEB refinement property are then automatically encoded in the Satisfiability Modulo Theory Library (SMT-LIB) language [3]. The resulting equivalence property is then checked using an SMT solver. Additional checks need to be performed to ensure that the NCL circuit is live (i.e., deadlock free). Thus, the overall verification has three high-level steps: (1) conversion from NCL to synchronous; (2) verification of converted synchronous against specification synchronous; and (3) additional checks on original NCL circuit to ensure liveness. The methodology can also be used to check the equivalence of two NCL circuits by applying the conversion technique to both NCL circuits to obtain two corresponding synchronous circuits, verifying these two synchronous circuits against each other, and performing the additional liveness checks on both NCL circuits.

## 15.2 Related verification works for asynchronous paradigms

Several formal verification techniques have been implemented to verify the two major asynchronous design paradigms: bounded-delay and QDI. The bounded-delay model is based on the assumption that the delay in all circuit components and

wires is bounded—i.e., worst case delay can be calculated. Because of these timing constraints, most of the verification schemes for timed asynchronous models involve trace theory, Signal Transition Graph [4], and timed Petri nets. Reference [5] illustrates a gate-level verification method based on trace theory where the circuit, as well as the correctness properties, is modeled as Petri nets. An approach based on time-driven unfolding of Petri nets is used to verify freedom from hazards in asynchronous circuits consisting of logic gates and micropipelines [6]. However, timed-model-based verification methods are not applicable to QDI circuits, which are based on exactly the opposite assumption that circuit delays are unbounded and therefore indeterminate.

There exist several verification schemes specific to QDI circuits as well. Verbeek and Schmaltz [7] illustrate a deadlock-verification scheme for QDI circuits based on the Click Library [8]. Circuits based on this primitive library are structurally different from other QDI paradigms, such as NCL. Moreover, this method does not verify the functional correctness (safety) of the circuit. Refinement-based formal methods have been successful in verifying both bounded-delay and QDI asynchronous models. Desynchronized circuits, which are based on a bounded-delay structure, can be verified by a refinement-based approach, as discussed in [9]. As mentioned in the previous section, reference [1] presents a method to check the functional equivalence of NCL circuits against their synchronous counterparts using WEB refinement; and a model-checking-based method that checks for safety and liveness of PCHB circuits is presented in [10]. However, both of these techniques suffer from state space explosion, since they model the QDI circuits as TSs, which become very complex for large circuits due to the nondeterministic behavior of QDI paradigms. Using a conversion technique along with WEB refinement, similar to that presented herein but applied to PCHB circuits, we were able to verify equivalence of combinational PCHB circuits with their Boolean specification, which proves to be highly scalable and much faster than previous techniques [11]. That method is currently being extended to sequential PCHB circuits.

AQ5

Along with safety and liveness, input-completeness and observability are two critical properties of NCL circuits, which must be verified in order to ensure delay insensitivity, since a circuit may function correctly under normal operating conditions while not being input-complete or observable, but may then malfunction under extreme timing scenarios, such as those caused by process, voltage, or temperature variations. A manual approach to checking input-completeness is outlined in [12], which requires an analysis of each output term. For example, in order for output  $Z$  to be input-complete with respect to input  $A$ , every product term in all rails of  $Z$  (in SOP format) must contain any rail of  $A$ . This ensures that  $Z$  cannot be DATA until  $A$  is DATA; and if  $Z$  is constructed solely out of NCL gates with hysteresis, the gate hysteresis ensures that  $Z$  cannot transition from DATA to NULL until  $A$  transitions from DATA to NULL. Hence,  $Z$  is input-complete with respect to  $A$ . However, this method cannot ensure input-completeness of relaxed NCL circuits [13], where not all gates contain hysteresis. Also, scalability is a problem with this approach, as the number of product terms that need to be verified

AQ6

grows exponentially as the number of inputs increase. Kondratyev *et al.* [14] provide a formal verification approach for observability verification, which entails determining all input combinations that assert  $gate_i$ , then forcing  $gate_i$  to remain de-asserted while checking that none of those input combinations result in all circuit outputs becoming DATA. This check is performed for all gates to ensure circuit observability; and if also applied to each circuit input (i.e., replace  $gate_i$  with  $input_i$  in the observability check explanation), it will guarantee input-completeness. Our approach for observability checking, detailed in Section 15.3.5, is very similar to [14], while our approach checks input-completeness for all inputs simultaneously, as detailed in Section 15.3.4.

### 15.3 Equivalence verification for combinational NCL circuits

In industry, asynchronous NCL circuits are typically synthesized from their synchronous counterparts. Throughout the synthesis and optimization process, the synchronous specification undergoes several transformations, resulting in major structural differences between the implemented NCL circuit and its synchronous specification. For this kind of scenario, equivalence checking is a widely used formal verification method that checks for logical and functional equivalence between two different circuits.

NCL verification based on equivalence checking has proved to be a unified, fast, and scalable approach that eliminates most of the limiting factors of previous verification works in the field. The NCL equivalence verification method requires five steps, as described below and detailed in the following subsections:

AQ7

- Step 1: The netlist of an NCL circuit to be verified is converted into a corresponding Boolean/synchronous netlist, which is modeled in the SMT-LIB language using an automated script that we developed. The converted netlist is then checked against its corresponding Boolean/synchronous specification using an SMT solver to test for functional equivalence, as detailed in Section 15.3.1.
- Step 2: Step 1 only checks the converted circuit's signals corresponding to the original NCL circuit's rail<sup>1</sup> signals, with their equivalent Boolean/synchronous specification external outputs or register outputs; hence, the original NCL circuit's rail<sup>0</sup> signals must also be ensured to be inverses of their respective rail<sup>1</sup> signals, through the invariant check detailed in Section 15.3.2, in order to guarantee safety after passing Step 1.
- Step 3: The NCL netlist is then automatically converted into a graph structure, and information related to the handshaking control is gathered by traversing the graph. This information is utilized to analyze the handshaking correctness of the circuit in order to check for deadlock, as detailed in Section 15.3.3.

Steps 4 and 5: Once the NCL circuit passes Step 2, each combinational logic (C/L) block must be verified to be both input-complete (Step 4) and observable (Step 5) in order to guarantee liveness of the circuit under all timing scenarios, as detailed in Sections 15.3.4 and 15.3.5, respectively.

### 15.3.1 Functional equivalence check

A  $3 \times 3$  NCL multiplier, shown in Figure 15.1(a), is used as an example to illustrate the equivalence verification procedure for combinational NCL circuits. NCL multipliers use input-incomplete NCL AND functions (denoted with an I inside the AND symbol), input-complete NCL AND functions (denoted with a C inside the AND symbol), NCL Half-Adders (HA), and NCL Full-Adders (FA), which all consist of a combination of NCL threshold gates, as shown in Figure 15.1(b), (c), (d), and (e), respectively. All signals in Figure 15.1(a) are dual-rail; and all registers are reset-to-NULL, denoted as REG\_NULL. In addition to the I/O registers, the multiplier in Figure 15.1(a) includes one intermediate register stage to increase throughput.

The netlist of the NCL  $3 \times 3$  multiplier is shown in Figure 15.2(a). The first two lines indicate all primary inputs and primary outputs, respectively. Lines 3–44 correspond to the NCL C/L threshold gates, where the first column is the type of gate, the second column lists the gate’s inputs, in comma separated format starting with input A, and the last column is the gate’s output. Lines 45–64 correspond to 1-bit NCL registers, where the first column is the reset type of the register (i.e., \_NULL, \_DATA0, or \_DATA1, for reset to NULL, DATA0, or DATA1, respectively), the second column denotes the register’s level (i.e., the depth of the path through registers without considering the C/L in-between. For the  $3 \times 3$  multiplier example, there are three stages of registers, with levels 1, 2, and 3, starting from the input registers), the third and fourth columns are the register’s rail<sup>0</sup> and rail<sup>1</sup> data inputs, respectively, the fifth and sixth columns are the register’s *Ki* input and *Ko* output, respectively, and the seventh and eighth columns are the register’s rail<sup>0</sup> and rail<sup>1</sup> data outputs, respectively. Lines 65–72 correspond to the C-elements (i.e., TH<sub>nn</sub> gates) used in the handshaking control circuitry, where the first column is *C<sub>n</sub>*, with *n* indicating the number of inputs to the C-element, the second column lists the inputs in comma separated format, and the last column is the C-element’s output. For example, C4 on line 65 is a four-input C-element.

The NCL netlist is input to a conversion algorithm that converts it into an equivalent Boolean netlist, as shown in Figure 15.2(b) for the Figure 15.2(a) example. Each NCL C/L gate is replaced with its corresponding Boolean gate that has the same set function, but no hysteresis; each internal dual-rail signal is already represented as two Boolean signals, the first for rail<sup>1</sup> and the second for rail<sup>0</sup>, so no changes are needed for these; and each primary dual-rail input is replaced with that signal’s rail<sup>1</sup>, as this corresponds to the equivalent Boolean signal. The rail<sup>1</sup> primary inputs are then inverted to produce internal signals corresponding to what

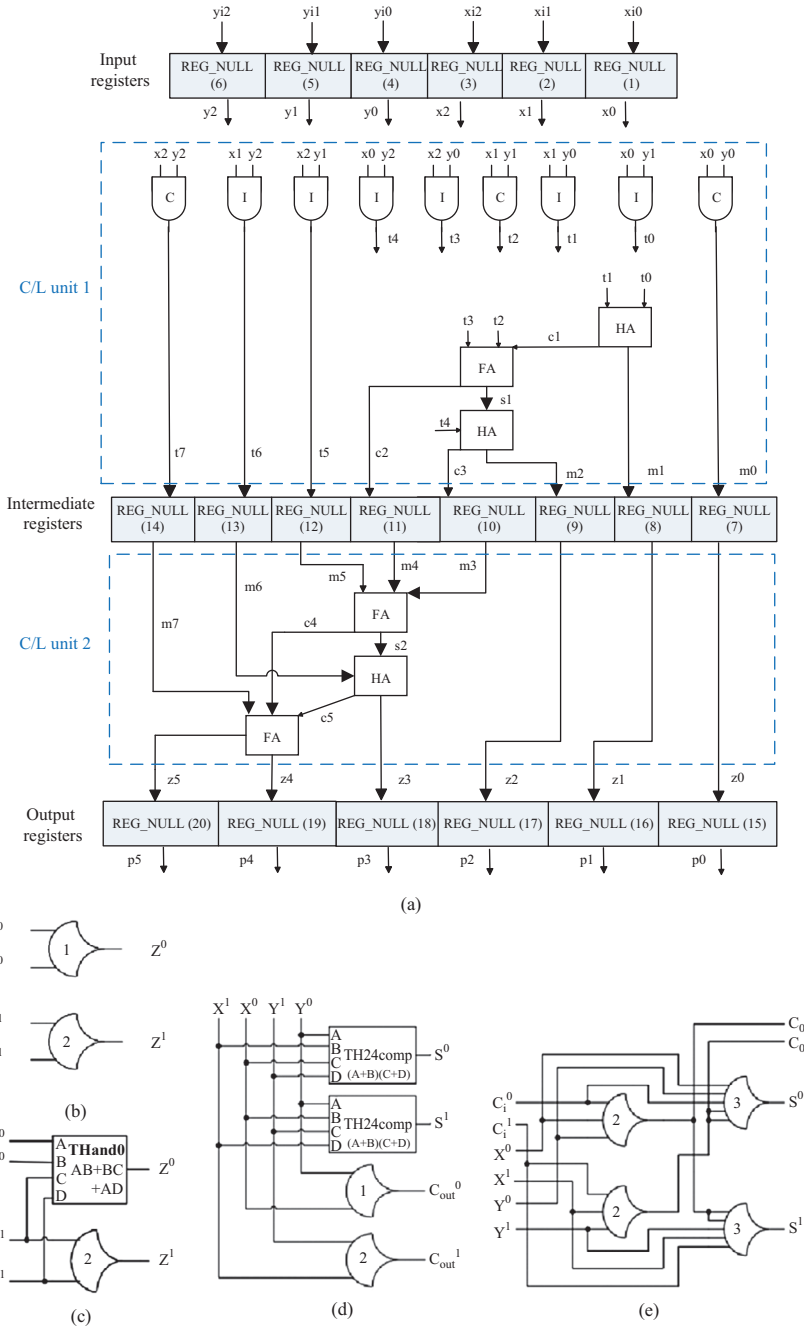


Figure 15.1 (a)  $3 \times 3$  NCL multiplier circuit. (b) Input-incomplete NCL AND. (c) Input-complete NCL AND. (d) NCL HA. (e) NCL FA

AQ8

<pre> 1. xi0_0,xi0_1,xi1_0,xi1_1,...,yi1_0,yi1_1,yi2_0,yi2_1 2. p0_0,p0_1,p1_0,p1_1,...,p5_0,p5_1 3. th22 x0_1,y0_1 m0_1 4. thand0 y0_0,x0_0,y0_1,x0_1 m0_0 5. th22 x0_1,y1_1 t0_1 6. th12 x0_0,y1_0 t0_0 7. th22 x0_1,y2_1 t4_1 8. th12 x0_0,y2_0 t4_0 9. th22 x1_1,y0_1 t1_1 10. th12 x1_0,y0_0 t1_0 11. th22 x1_1,y1_1 t2_1 12. thand0 y1_0,x1_0,y1_1,x1_1 t2_0 13. th22 x1_1,y2_1 t6_1 14. th12 x1_0,y2_0 t6_0 15. th22 x2_1,y0_1 t3_1 16. th12 x2_0,y0_0 t3_0 17. th22 x2_1,y1_1 t5_1 18. th12 x2_0,y1_0 t5_0 19. th22 x2_1,y2_1 t7_1 20. thand0 y2_0,x2_0,y2_1,x2_1 t7_0 21. th24comp t0_0,t1_0,t0_1,t1_1 m1_1 22. th24comp t0_0,t1_1,t1_0,t0_1 m1_0 23. th22 t0_1,t1_1 c1_1 24. th12 t0_0,t1_0 c1_0 25. th23 t3_0,t2_0,c1_0 c2_0 26. th23 t3_1,t2_1,c1_1 c2_1 27. th34w2 c2_0,t3_1,t2_1,c1_1 s1_1 28. th34w2 c2_1,t3_0,t2_0,c1_0 s1_0 29. th24comp s1_0,t4_0,s1_1,t4_1 m2_1 30. th24comp s1_0,t4_1,t4_0,s1_1 m2_0 31. th22 s1_1,t4_1 c3_1 32. th12 s1_0,t4_0 c3_0 33. th23 m5_0,m4_0,m3_0 c4_0 34. th23 m5_1,m4_1,m3_1 c4_1 35. th34w2 c4_0,m5_1,m4_1,m3_1 s2_1 36. th34w2 c4_1,m5_0,m4_0,m3_0 s2_0 37. th24comp s2_0,m6_0,s2_1,m6_1 z3_1 38. th24comp s2_0,m6_1,m6_0,s2_1 z3_0 39. th22 s2_1,m6_1 c5_1 40. th12 s2_0,m6_0 c5_0 41. th23 m7_0,c4_0,c5_0 z5_0 42. th23 m7_1,c4_1,c5_1 z5_1 43. th34w2 z5_0,m7_1,c4_1,c5_1 z4_1 44. th34w2 z5_1,m7_0,c4_0,c5_0 z4_0 45. Reg_NULL 1 xi0_0 xi0_1 KO3 ko1 x0_0 x0_1 46. Reg_NULL 1 xi1_0 xi1_1 KO3 ko2 x1_0 x1_1 47. Reg_NULL 1 xi2_0 xi2_1 KO3 ko3 x2_0 x2_1 48. Reg_NULL 1 yi0_0 yi0_1 KO3 ko4 y0_0 y0_1 49. Reg_NULL 1 yi1_0 yi1_1 KO3 ko5 y1_0 y1_1 50. Reg_NULL 1 yi2_0 yi2_1 KO3 ko6 y2_0 y2_1 51. Reg_NULL 2 m0_0 m0_1 ko15 ko7 z0_0 z0_1 52. Reg_NULL 2 m1_0 m1_1 ko16 ko8 z1_0 z1_1 53. Reg_NULL 2 m2_0 m2_1 ko17 ko9 z2_0 z2_1 54. Reg_NULL 2 c3_0 c3_1 KO4 ko10 m3_0 m3_1 55. Reg_NULL 2 c2_0 c2_1 KO4 ko11 m4_0 m4_1 56. Reg_NULL 2 t5_0 t5_1 KO4 ko12 m5_0 m5_1 57. Reg_NULL 2 t6_0 t6_1 KO4 ko13 m6_0 m6_1 58. Reg_NULL 2 t7_0 t7_1 KO5 ko14 m7_0 m7_1 59. Reg_NULL 3 z0_0 z0_1 Ki ko15 p0_0 p0_1 60. Reg_NULL 3 z1_0 z1_1 Ki ko16 p1_0 p1_1 61. Reg_NULL 3 z2_0 z2_1 Ki ko17 p2_0 p2_1 62. Reg_NULL 3 z3_0 z3_1 Ki ko18 p3_0 p3_1 63. Reg_NULL 3 z4_0 z4_1 Ki ko19 p4_0 p4_1 64. Reg_NULL 3 z5_0 z5_1 Ki ko20 p5_0 p5_1 65. C4 ko7,ko8,ko9,ko10 KO1 66. C4 ko11,ko12,ko13,ko14 KO2 67. C2 KO1,KO2 KO3 68. C3 ko18,ko19,ko20 KO4 69. C2 ko19,ko20 KO5 70. C3 ko4,ko5,ko6 KO6 71. C3 ko1,ko2,ko3 KO7 72. C2 KO7,KO6 KO </pre>	<pre> 1. xi0_1,xi1_1,xi2_1,yi0_1,yi1_1,yi2_1 2. p0_0,p0_1,p1_0,p1_1,...,p5_0,p5_1 3. not xi0_1 xi0_0 4. not xi1_1 xi1_0 5. not xi2_1 xi2_0 6. not yi0_1 yi0_0 7. not yi1_1 yi1_0 8. not yi2_1 yi2_0 9. th22 xi0_1,yi0_1 p0_1 10. thand0 yi0_0,xi0_0,yi0_1,xi0_1 p0_0 11. th22 xi0_1,yi1_1 t0_1 12. th12 xi0_0,yi1_0 t0_0 13. th22 xi0_1,yi2_1 t4_1 14. th12 xi0_0,yi2_0 t4_0 15. th22 xi1_1,yi0_1 t1_1 16. th12 xi1_0,yi0_0 t1_0 17. th22 xi1_1,yi1_1 t2_1 18. thand0 yi1_0,xi1_0,yi1_1,xi1_1 t2_0 19. th22 xi1_1,yi2_1 t6_1 20. th12 xi1_0,yi2_0 t6_0 21. th22 xi2_1,yi0_1 t3_1 22. th12 xi2_0,yi0_0 t3_0 23. th22 xi2_1,yi1_1 t5_1 24. th12 xi2_0,yi1_0 t5_0 25. th22 xi2_1,yi2_1 t7_1 26. thand0 yi2_0,xi2_0,yi2_1,xi2_1 t7_0 27. th24comp t0_0,t1_0,t0_1,t1_1 p1_1 28. th24comp t0_0,t1_1,t1_0,t0_1 p1_0 29. th22 t0_1,t1_1 c1_1 30. th12 t0_0,t1_0 c1_0 31. th23 t3_0,t2_0,c1_0 c2_0 32. th23 t3_1,t2_1,c1_1 c2_1 33. th34w2 c2_0,t3_1,t2_1,c1_1 s1_1 34. th34w2 c2_1,t3_0,t2_0,c1_0 s1_0 35. th24comp s1_0,t4_0,s1_1,t4_1 p2_1 36. th24comp s1_0,t4_1,t4_0,s1_1 p2_0 37. th22 s1_1,t4_1 c3_1 38. th12 s1_0,t4_0 c3_0 39. th23 t5_0,c2_0,c3_0 c4_0 40. th23 t5_1,c2_1,c3_1 c4_1 41. th34w2 c4_0,t5_1,c2_1,c3_1 s2_1 42. th34w2 c4_1,t5_0,c2_0,c3_0 s2_0 43. th24comp s2_0,t6_0,s2_1,t6_1 p3_1 44. th24comp s2_0,t6_1,t6_0,s2_1 p3_0 45. th22 s2_1,t6_1 c5_1 46. th12 s2_0,t6_0 c5_0 47. th23 t7_0,c4_0,c5_0 p5_0 48. th23 t7_1,c4_1,c5_1 p5_1 49. th34w2 p5_0,t7_1,c4_1,c5_1 p4_1 50. th34w2 p5_1,t7_0,c4_0,c5_0 p4_0 </pre>
--	---

(a)

(b)

Figure 15.2 (a)  $3 \times 3$  NCL multiplier netlist. (b) Converted Boolean netlist

used to be the rail<sup>0</sup> primary inputs, as these are utilized in the internal logic. The first two lines in the converted netlist are the list of primary inputs and outputs, respectively, where the inputs correspond to the original NCL netlist's rail<sup>1</sup> inputs, and the outputs include both rail<sup>0</sup> and rail<sup>1</sup> outputs. Lines 3–8 in the converted netlist are the added inverters used to produce the equivalent signals to the original rail<sup>0</sup> inputs, as these were removed in the conversion. The format of each gate is the same as explained above for the NCL netlist. All *Reg\_NULL* components are removed during conversion by setting their data outputs equal to their data inputs, since these have no corresponding functionality in the equivalent Boolean circuit. Purely C/L circuits will not include *Reg\_DATA* components, as these correspond to synchronous registers; these will be discussed in Section 15.4.

The converted Boolean netlist is automatically encoded in the SMT-LIB language [3], using a conversion tool we developed, which is then input to an SMT solver to check for functional equivalence with the corresponding specification. For the  $3 \times 3$  multiplier example, the SMT solver checks for the following safety property:  $F_{\text{NCL\_Bool\_Equiv.}}(x2\_I, x1\_I, x0\_I, y2\_I, y1\_I, y0\_I) = \text{MUL}(x, y)$ , where  $(x2\_I, x1\_I, x0\_I)$  and  $(y2\_I, y1\_I, y0\_I)$  are the  $x$  and  $y$  rail<sup>1</sup> inputs, respectively, starting with the MSB. We use the Z3 SMT solver [15] to check for equivalence, but any combinational equivalence checker could be used. Note that only the rail<sup>1</sup> outputs need to be checked here, as these correspond to the Boolean specification circuit outputs. The rail<sup>0</sup> outputs will be utilized for the invariant check, described next.

AQ9

### 15.3.2 Invariant check

Since only the rail<sup>1</sup> outputs are utilized for the functional equivalence check, the rail<sup>0</sup> outputs must also be checked to ensure safety. To address correctness of the rail<sup>0</sup> outputs, an additional SMT invariant proof obligation is required for the original NCL circuit, which states that in any reachable NCL circuit state where the outputs are all DATA, every rail<sup>0</sup> output must be the inverse of its corresponding rail<sup>1</sup> output.

One way to achieve this is to initialize all registers to NULL, all C/L gate outputs to 0, and all register  $Ki$  inputs to  $rfd$  (i.e., logic 1), then make all the primary inputs DATA (i.e., represented in SMT as all combinations of valid DATA) and step the circuit. This will allow the input DATA to flow through all stages of the circuit, generating all possible combinations of valid DATA at the primary outputs. For each primary dual-rail output, the invariant is then checked to ensure that the rail<sup>0</sup> output is the inverse of its corresponding rail<sup>1</sup> output. For a C/L circuit with  $j$  registers  $r^1, \dots, r^j$ ,  $k$  C/L threshold gates  $g^1, \dots, g^k$ ,  $q$  dual-rail inputs  $i^1, \dots, i^q$ , and  $l$  dual-rail outputs  $o^l \langle R^0, R^1 \rangle, \dots, o^l \langle R^0, R^1 \rangle$ , where  $R^0$  and  $R^1$  are the output's rail<sup>0</sup> and rail<sup>1</sup>, respectively, the proof obligation for this invariant check is shown below as Proof Obligation 1. Predicate  $P1$  indicates that all registers in are reset-to-NULL.  $P2$  and  $P3$  state that all threshold gates and  $Ki$  register inputs are initialized to logic 0 and 1, respectively.  $P4$  indicates that all inputs are DATA.  $P5$  represents



the symbolic step of the circuit with all threshold gates set to 0 and all inputs set to DATA, with the new values of the threshold gates stored in  $(g_B^1, \dots, g_B^k)$ . *P6* states that the rails of each dual-rail output are complements of each other. The proof obligation, *PO1*, indicates that if DATA is allowed to flow from the primary inputs to the primary outputs, then for all possible valid DATA inputs, each output's rail<sup>0</sup>,  $R^0$ , is always the inverse of its respective rail<sup>1</sup> output,  $R^1$ .

*Proof Obligation 1:*

$$P1: \bigwedge_{n=1}^j (r_A^n = 0b00)$$

$$P2: \bigwedge_{n=1}^k (g_A^n = 0)$$

$$P3: \bigwedge_{n=1}^j (Ki_A^n = 1)$$

$$P4: \bigwedge_{n=1}^q (i_A^n = 0b01) \vee (i_A^n = 0b10)$$

$$P5: (g_B^1, \dots, g_B^k) = NCLStep(i_A^1, \dots, i_A^q)$$

$$P6: \bigwedge_{n=1}^n o_B^n \langle R^0 \rangle = \neg o_B^n \langle R^1 \rangle$$

$$PO1: \{P1 \wedge P2 \wedge P3 \wedge P4 \wedge P5 \Rightarrow P6\}$$

An alternative, faster method to check invariants is to check each NCL circuit stage independently. To do this, we developed an algorithm that reads the original NCL circuit netlist and separately extracts each circuit stage. Then, for each extracted stage, we set all gate outputs to 0, all stage inputs to DATA, and step the circuit, such that the stage's outputs become all possible combinations of valid DATA. Finally, the invariant is checked for each of the stage's dual-rail outputs to ensure that its rail<sup>0</sup> is the inverse of its corresponding rail<sup>1</sup>. The proof obligation for this second invariant check method is shown below as Proof Obligation 2, where the extracted stage has  $j$  dual-rail inputs  $i^1, \dots, i^j$ ,  $m$  threshold gates  $g^1, \dots, g^m$ , and  $k$  dual-rail outputs  $o^1 \langle R^0, R^1 \rangle, \dots, o^k \langle R^0, R^1 \rangle$ , where  $R^0$  and  $R^1$  are the output's rail<sup>0</sup> and rail<sup>1</sup>, respectively. Predicate *P1* indicates that all stage inputs are valid DATA; *P2* indicates that all NCL threshold gates in the stage are initialized to 0; *P3* corresponds to a NULL to DATA transition of the stage; and *P4* states that the rails of each dual-rail output are complements of each other. The Proof Obligation, *PO2*, states that after a NULL to DATA transition of the stage with all possible valid DATA inputs, that each output's rail<sup>0</sup>,  $R^0$ , is always the inverse of its respective rail<sup>1</sup> output,  $R^1$ .

*Proof Obligation 2:*

$$P1: \bigwedge_{n=1}^j (i_A^n = 0b01) \vee (i_A^n = 0b10)$$

$$P2: \bigwedge_{n=1}^m (g_A^n = 0)$$

$$P3: (g_B^1, \dots, g_B^m) = NCLStep(i_A^1, \dots, i_A^j)$$

$$P4: \bigwedge_{n=1}^k o_B^n \langle R^0 \rangle = \neg o_B^n \langle R^1 \rangle$$

$$PO2: \{P1 \wedge P2 \wedge P3 \Rightarrow P4\}$$

This second invariant check method is much faster than the first, since it breaks the problem into a set of smaller invariant checks (i.e., one per stage), whereas the first method checks the invariant for the entire circuit all at once. For example,

Method 2 is 38% faster for a two-stage  $10 \times 10$  multiplier, and becomes even faster when the circuit includes additional stages. Note that for both invariant check methods, the NCL gates are modeled in SMT as Boolean functions (i.e., no hysteresis), since invariant checking only requires the NULL to DATA transition, which only utilizes each gate's set function, that is, the same for the Boolean and NCL state-holding gate implementations. This optimization reduces the invariant check time by approximately half (e.g., 377 vs. 192 s for a non-pipelined 10-bit  $\times$  10-bit unsigned multiplier).

### 15.3.3 Handshaking check

Liveness means absence of deadlock in a circuit. For combinational NCL circuits, proper connections between handshaking signals, along with observable and input-complete C/L, ensures liveness. The same NCL netlist shown in Figure 15.2(a), used as input for the functional equivalence and invariant checks, is also utilized as input for the liveness checks. For the handshaking check, the NCL netlist is automatically converted into a graph structure, and the handshaking paths and C-element connections are traced back to verify proper handshaking, ensuring that every register acknowledges all preceding stage register outputs that took part in calculating its input. For each NCL register,  $i$ , its dual-rail input is traced back through its preceding C/L to identify every NCL register's dual-rail output that took part in its calculation, generating a fan-in list,  $reg\_fanin(i)$ . For example, referring to Figure 15.1(a),  $reg\_fanin(8)$  would be 1, 2, 4, 5, since  $x0$ ,  $x1$ ,  $y0$ , and  $y1$  are all used to generate  $m1$ . Also, for each NCL register,  $i$ , its  $Ko$  output is traced through the C-element handshaking circuitry to identify every NCL register's  $Ki$  input that register  $i$ 's  $Ko$  output took part in calculating, generating a  $Ko$  fanout list,  $ko\_fanout(i)$ . For example, referring to Figure 15.3, which shows the handshaking circuitry for the  $3 \times 3$  multiplier example,  $ko\_fanout(8)$  would be 1, 2, 3, 4, 5, 6, since  $ko8$  takes part in the generation of the  $Ki$  input for all of the preceding stage's registers (i.e., 1–6).

After  $reg\_fanin$  and  $ko\_fanout$  for each NCL register is calculated, as shown in Figure 15.4 for the  $3 \times 3$  multiplier example,  $reg\_fanin(k)$  is checked to ensure that it is a subset of  $ko\_fanout(k)$ , for all NCL registers. Note that 0 in  $reg\_fanin$  denotes a primary data input; and 0 in  $ko\_fanout$  denotes the external  $Ko$  output. Bit-wise completion results in  $reg\_fanin(k)$  being equal to  $ko\_fanout(k)$ , while full-word completion results in  $reg\_fanin(k)$  being a proper subset of  $ko\_fanout(k)$ , with the restriction that each register that is in  $ko\_fanout(k)$  and not in  $reg\_fanin(k)$  must be from the immediate preceding register stage of register  $k$ .  $reg\_fanin(k)$  not being a subset of  $ko\_fanout(k)$  could result in deadlock, while  $reg\_fanin(k)$  being a proper subset of  $ko\_fanout(k)$  but violating the stage restriction described above, could either result in deadlock or may just decrease circuit performance. Hence, if  $reg\_fanin(k)$  is a proper subset of  $ko\_fanout(k)$ , then each register that is in  $ko\_fanout(k)$  and not in  $reg\_fanin(k)$  is automatically inspected to ensure that it meets this stage restriction. If not, a warning message is generated denoting the

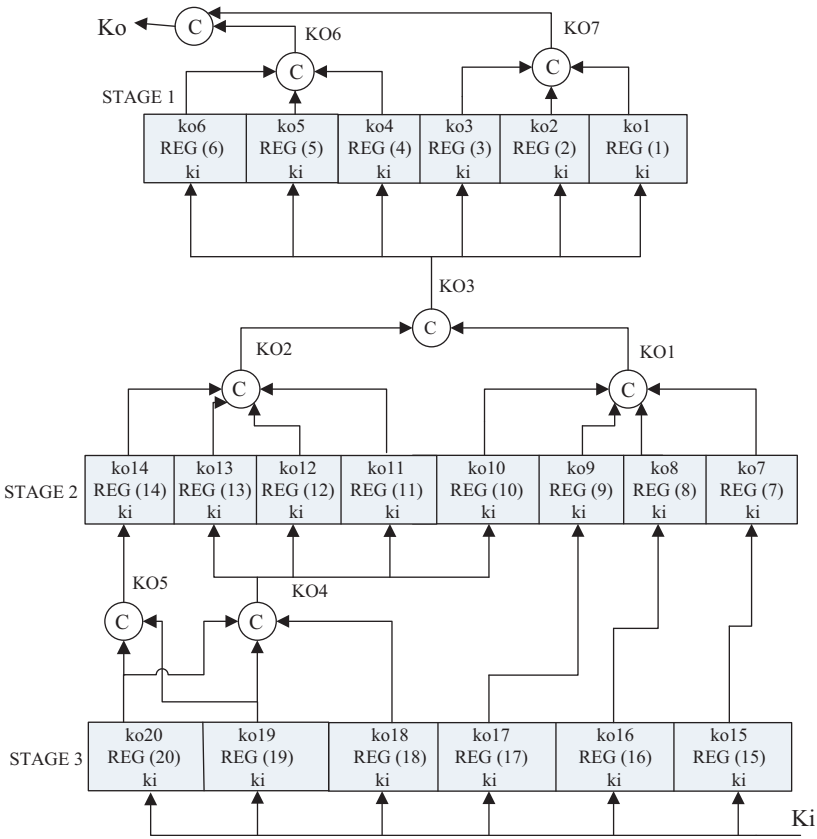


Figure 15.3 Handshaking connections for the  $3 \times 3$  NCL multiplier

extra register in that particular register’s *ko\_fanout* list, to allow for easier manual inspection. For the Figure 15.3 example, the first stage utilizes full-word completion, while the second stage uses bit-wise completion.

An additional check is needed to ensure correct connection of the external *Ki* input, namely that the external *Ki* should be the *Ki* input to every register that produces a primary data output. The developed algorithm generates an appropriate descriptive error message in case the NCL circuit fails to satisfy any of these handshaking checks. Furthermore, it checks to ensure that no data signal is part of the handshaking circuitry, and that no handshaking signal is part of a data signal.

The methodology has been demonstrated on several multipliers and ISCAS-85 [16] combinational circuit benchmarks, as shown in Table 15.1. *umultN* represents a non-pipelined  $N$ -bit  $\times$   $N$ -bit unsigned multiplier. The NCL-to-Boolean netlist conversion time was negligible compared to the safety and invariant checks

1: reg_fanin: 0	ko_fanout: 0
2: reg_fanin: 0	ko_fanout: 0
3: reg_fanin: 0	ko_fanout: 0
4: reg_fanin: 0	ko_fanout: 0
5: reg_fanin: 0	ko_fanout: 0
6: reg_fanin: 0	ko_fanout: 0
7: reg_fanin: [1, 4]	ko_fanout: [1, 2, 3, 4, 5, 6]
8: reg_fanin: [1, 2, 4, 5]	ko_fanout: [1, 2, 3, 4, 5, 6]
9: reg_fanin: [1, 2, 3, 4, 5, 6]	ko_fanout: [1, 2, 3, 4, 5, 6]
10: reg_fanin: [1, 2, 3, 4, 5, 6]	ko_fanout: [1, 2, 3, 4, 5, 6]
11: reg_fanin: [1, 2, 3, 4, 5]	ko_fanout: [1, 2, 3, 4, 5, 6]
12: reg_fanin: [3, 5]	ko_fanout: [1, 2, 3, 4, 5, 6]
13: reg_fanin: [2, 6]	ko_fanout: [1, 2, 3, 4, 5, 6]
14: reg_fanin: [3, 6]	ko_fanout: [1, 2, 3, 4, 5, 6]
15: reg_fanin: [7]	ko_fanout: [7]
16: reg_fanin: [8]	ko_fanout: [8]
17: reg_fanin: [9]	ko_fanout: [9]
18: reg_fanin: [10, 11, 12, 13]	ko_fanout: [10, 11, 12, 13]
19: reg_fanin: [10, 11, 12, 13, 14]	ko_fanout: [10, 11, 12, 13, 14]
20: reg_fanin: [10, 11, 12, 13, 14]	ko_fanout: [10, 11, 12, 13, 14]

Figure 15.4 *reg\_fanin* and *ko\_fanout* lists for the  $3 \times 3$  NCL multiplierTable 15.1 *Verification results of various C/L NCL circuits*

Circuits	Functional check (s)	Invariant check (s)	Handshaking check (s)	Total time (s)
<i>ISCAS c17</i>	0.01	0.01	0.0020	0.0220
<i>umult2</i>	0.02	0.01	0.0997	0.1297
<i>umult3</i>	0.04	0.02	0.1087	0.1687
<i>umult6</i>	0.32	0.33	0.8238	1.4738
<i>umult8</i>	10.62	6.79	9.3090	26.719
<i>umult10</i>	683.49	192.39	70.370	946.25
<i>ISCAS c432</i>	1.03	1.06	3.0111	5.1011
<i>umult10-B1</i>	0.08 (B)	0.10 (B)	70.370	70.550
<i>umult10-B2</i>	0.06 (B)	192.39	70.370	262.82
<i>umult10-B3</i>	683.49	192.39	69.1538 (B)	945.034
<i>umult10-B4</i>	683.49	0.08 (B)	72.0235 (B)	755.5935
<i>umult10-B5</i>	0.1 (B)	0.09 (B)	70.37	71.37

performed by the Z3 SMT solver [15] on an Intel<sup>®</sup> Core<sup>™</sup> i7-4790 CPU with 32GB of RAM, running at 3.60 GHz. To test the methodology, we injected several bugs. The *umult10-Bn* multipliers are circuits with  $n$  different kinds of bugs, and the (B) in either the Functional Check, Invariant check, or Handshaking Check column denotes which check detected the bug. The -B1 bug incorrectly swaps rails of a dual-rail signal. -B2 represents a faulty data connection. For example, the  $F$  output of NCL *gate<sub>i</sub>* should be connected to the  $X$  input of NCL *gate<sub>j</sub>*; however,  $X$  is

instead connected to the output of NCL  $gate_k$ , which results in a logical error. –B3 corresponds to an incorrect handshaking connection; and external  $Ki$  and  $Ko$  bugs are represented by –B4. –B5 denotes a rail-duplication error, where  $rail^0$  and  $rail^1$  of a particular signal are the same wire. Z3 reported all functional and invariant bugs along with a counter example; and our handshaking check tool identified and reported the location of all inserted completion logic bugs.

### 15.3.4 Input-completeness check

Input-completeness requires that all outputs of a combinational circuit may not transition from NULL to DATA until all inputs have transitioned from NULL to DATA, and that all outputs of a combinational circuit may not transition from DATA to NULL until all inputs have transitioned from DATA to NULL [12]. In circuits with multiple outputs, it is acceptable according to Seitz’s “weak conditions” of delay-insensitive signaling, for some of the outputs to transition without having a complete input set present, as long as all outputs cannot transition before all inputs arrive [17]. Input-completeness of every C/L stage is required for NCL circuits to be QDI; an input-incomplete stage may cause the circuit to deadlock under some timing scenarios.

There are two proof obligations required for verification of input-completeness. These two proof obligations have been developed to accommodate two scenarios, the first for when the circuit transitions from NULL to DATA, and the second for the transition from DATA to NULL. Both proof obligations have been generalized so that they apply to all NCL combinational circuits. The proof obligations have been encoded in a decidable fragment of first-order logic, and are automatically checked using an SMT solver.

#### 15.3.4.1 Input-completeness proof obligation: NULL to DATA

Assume an NCL circuit has  $m$  threshold gates,  $p$  dual-rail-inputs, and  $q$  dual-rail outputs. Let  $g_A^1, \dots, g_A^m$  represent Boolean variables that correspond to the current state of the NCL threshold gates before *step A*, and  $g_B^1, \dots, g_B^m$  represent the same threshold gates’ state after *step A*. Let  $i_A^1, \dots, i_A^p$  represent the circuit inputs for *step A*, and  $i_B^1, \dots, i_B^p$  for *step B*. Let  $o_A^1, \dots, o_A^q$  be the circuit output values after symbolically stepping the circuit using inputs  $i_A^1, \dots, i_A^p$  and threshold gate states  $g_A^1, \dots, g_A^m$ . Let  $o_B^1, \dots, o_B^q$  be the circuit output values after symbolically stepping the circuit using inputs  $i_B^1, \dots, i_B^p$  and threshold gate states  $g_B^1, \dots, g_B^m$ . The predicates used in the proof obligations for input-completeness are given in Table 15.2.

$p_0$  indicates that no dual-rail inputs are in an illegal state.  $p_1$  states that all the threshold gate’s current output values are 0, which indicates that the circuit is in the NULL state before a DATA transition.  $p_2$  indicates that at least one of the dual rail inputs is NULL, and  $p_3$  indicates that at least one of the dual-rail outputs is NULL. Proof Obligation *PO3*, below, is used to check input-completeness of the NULL to DATA transition of the circuit. *PO3* essentially states that if none of the inputs are ILLEGAL, all current threshold gate outputs are 0, and at least one of the dual-rail

Table 15.2 *Proof obligation predicates for input-completeness*

$p_n$	Predicate
$p_0$	$\bigwedge_{n=1}^{n=p} \sim (i_A^n = 0b11)$
$p_1$	$\bigwedge_{n=1}^{n=m} (g_A^n = 0)$
$p_2$	$\bigvee_{n=1}^{n=p} (i_A^n = 0b00)$
$p_3$	$\bigvee_{n=1}^{n=q} (o_A^n = 0b00)$
$p_4$	$\bigwedge_{n=1}^{n=p} ((i_A^n = 0b01) \vee (i_A^n = 0b10))$
$p_5$	$(g_B^1, \dots, g_B^m) = NCLStep(i_A^1, \dots, i_A^p)$
$p_6$	$\bigwedge_{n=1}^{n=p} ((i_B^n = i_A^n) \vee (i_B^n = 0b00))$
$p_7$	$\bigvee_{n=1}^{n=p} (i_B^n = i_A^n)$
$p_8$	$\bigvee_{n=1}^{n=q} ((o_B^n = 0b01) \vee (o_B^n = 0b10))$

inputs is NULL, then at least one of the dual-rail outputs must be NULL. Since the dual-rail inputs in the proof obligation are symbolic, the SMT solver checks this property for all possible input combinations.

$$PO3: \{p_0 \wedge p_1 \wedge p_2\} \rightarrow p_3$$

#### 15.3.4.2 Input-completeness proof obligation: DATA to NULL

When NCL circuits are constructed using only threshold gates with hysteresis, ensuring input-completeness of the NULL to DATA transition guarantees input-completeness of the DATA to NULL transition, since gate hysteresis ensures that a gate output cannot transition to 0 until all its inputs transition to 0. However, this is not the case for relaxed NCL circuits [13], which are comprised of both threshold gates with hysteresis and Boolean gates. Hence, for relaxed NCL circuits, input-completeness of the DATA to NULL transition must also be checked.

To formulate the DATA to NULL proof obligation, the circuit must first be symbolically initialized with all possible threshold gate outputs after a transition from NULL to DATA. This is done by first initializing the circuit to the NULL state (i.e., all threshold gates are set to 0) and then stepping the circuit with valid symbolic DATA (i.e., not NULL and not illegal) inputs, identified as *step A*.

The symbolic values of the threshold gates from *step A* are retained, and the circuit is symbolically stepped again with new inputs, identified as *step B*, which represents the DATA to NULL transition.

$p_1$  initializes all threshold gate outputs to 0 before *step A*.  $p_4$  indicates that all *step A* inputs are DATA.  $p_5$  represents the symbolic step of the circuit with all threshold gates set to 0 and all inputs set to DATA, with the new values of the threshold gates stored in  $(g_B^1, \dots, g_B^m)$ .  $p_6$  indicates that each input for *step B* is either the same DATA value it was for *step A*, or has transitioned to NULL.  $p_7$  indicates that at least one of the inputs for *step B* is still DATA; and  $p_8$  indicates that at least one of the outputs of *step B* remains DATA. The final proof obligation for input-completeness of the DATA to NULL transition is given below as *PO4*. It states that after initializing the circuit to the NULL state and symbolically stepping the circuit with all possible DATA inputs to generate all possible DATA states, that if at least one dual-rail input remains DATA while other inputs may transition to NULL, then at least one of the outputs must remain DATA, meaning that the circuit has not fully transitioned to the NULL state, because all inputs have not yet transitioned to NULL. Like the NULL to DATA proof obligation, all inputs are symbolic, so the SMT solver checks all combinations.

$$PO4: \{p_1 \wedge p_4 \wedge p_5 \wedge p_6 \wedge p_7\} \rightarrow p_8$$

### 15.3.4.3 Input-completeness results

Verification of the proof obligations for input-completeness can be performed using any SMT solver. To perform input-completeness verification, we developed a tool to automatically generate the circuit model and proof obligation specifications, encoded in SMT-LIB format, from the original circuit netlist, such as the one shown in Figure 15.2(a) for the  $3 \times 3$  multiplier. For the verification results presented here,  $N$ -bit  $\times$   $N$ -bit unsigned dual-rail NCL multipliers were used as benchmarks, where  $3 \leq N \leq 15$ . The ISCAS-85 C432 27-channel interrupt controller circuit was also used as a benchmark [18]. The verification proof obligations were checked using the Z3 SMT solver on an Intel® Core™ i7-4790 CPU with 32GB of RAM, running at 3.60 GHz.

The verification results are listed in Table 15.3, where the first column is the Circuit Name, the second column is the verification time for the NULL to DATA proof obligation of a correct input-complete implementation, the third column is the verification time for the NULL to DATA proof obligation of an incorrect input-incomplete implementation, and columns four and five report the verification times for the DATA to NULL proof obligations for input-complete and input-incomplete implementations, respectively. *umultN* represents an  $N$ -bit  $\times$   $N$ -bit unsigned multiplier constructed using only NCL gates with hysteresis, while *r - umultN* represents a relaxed version of the  $N$ -bit  $\times$   $N$ -bit multiplier, where NCL gates are replaced with Boolean gates when hysteresis is not required for input-completeness. Timeout (TO) is listed in the verification results when the verification time exceeded 1 day.

Table 15.3 *Input-completeness verification times (s)*

Circuit	N to D	Buggy N to D	D to N	Buggy D to N
<i>umult3</i>	0.02	0.01	0.03	0.04
<i>umult4</i>	0.02	0.05	0.06	0.06
<i>umult5</i>	0.09	0.05	0.12	0.11
<i>umult6</i>	0.11	0.15	0.38	0.24
<i>umult7</i>	0.38	0.27	1.49	1.23
<i>umult8</i>	1.44	0.49	5.47	3.60
<i>umult9</i>	5.30	2.37	22.38	1.28
<i>umult10</i>	20.22	8.92	102.42	18.45
<i>umult11</i>	54.09	2.99	430.29	22.81
<i>umult12</i>	236.00	8.21	1,909.44	23.17
<i>umult13</i>	885.30	3.85	7,401.11	15.11
<i>umult14</i>	3,424.89	114.41	34,961.6	8.26
<i>umult15</i>	9,663.01	19.41	<b>TO</b>	112.55
<i>r - umult3</i>	0.02	0.02	0.04	0.07
<i>r - umult4</i>	0.02	0.02	0.06	0.07
<i>r - umult5</i>	0.05	0.04	0.10	0.08
<i>r - umult6</i>	0.15	0.12	0.42	0.07
<i>r - umult7</i>	0.39	0.12	1.48	0.11
<i>r - umult8</i>	1.38	1.43	6.38	0.17
<i>r - umult9</i>	4.74	5.17	28.03	0.20
<i>r - umult10</i>	16.26	19.02	146.95	0.20
<i>r - umult11</i>	58.04	46.53	642.80	0.31
<i>r - umult12</i>	215.75	228.47	3,635.01	0.35
<i>r - umult13</i>	729.11	34.97	15,663.24	0.40
<i>r - umult14</i>	3,045.99	4,104.45	80,213.90	0.68
<i>r - umult15</i>	10,561.11	9,974.39	<b>TO</b>	0.308
C432	0.062	0.068	0.074	0.94

The benchmark multipliers were designed as shown for the  $3 \times 3$  version in Figure 15.1, with input-complete AND functions to generate the  $X_i Y_i$  partial products and input-incomplete AND functions for the  $X_i Y_j$  partial products, where  $i \neq j$ , but without the intermediate NCL register (i.e., a single stage with only input and output registers [19]). To create the buggy non-relaxed versions,  $1 \leq k \leq N$  was chosen at random and the input-complete AND function used to generate the  $X_k Y_k$  partial product was replaced with an input-incomplete version. NCL HAs and FAs are inherently input-complete and therefore cannot be made input-incomplete when constructed only using NCL gates with hysteresis. The relaxed version of each multiplier was constructed by taking the non-relaxed version and replacing the TH22 gate within the input-incomplete AND functions and HAs with a Boolean AND gate. Buggy relaxed circuits were constructed by relaxing one of the following: either the TH22 or THand0 gate in a  $X_i Y_i$  partial product AND function, a TH24comp gate in a HA, or either a TH34w2 or TH23 gate in a FA. The ISCAS-85 C432 circuit was designed using input-incomplete functions when possible while



maintaining input-completeness. The buggy version was obtained by replacing one of the input-complete 3-input NAND functions that calculate RC, in Module M3 [20], with an input-incomplete version. Z3 reported all bugs along with a counter example.

### 15.3.5 Observability check

Observability requires every gate transition to be observable at the output, which means that every gate that transitions is necessary to transition at least one output. Observability of every gate in every C/L stage is required for NCL circuits to be QDI; an unobservable gate in any stage may cause the circuit to deadlock under some timing scenarios. Observability can be proven in a similar fashion to input-completeness. Two proof obligations are needed for each C/L gate, one for the NULL to DATA transition, and the other for the DATA to NULL transition. The proof obligations, like those for input-completeness, have been encoded in a decidable fragment of first order logic and are automatically checked using an SMT solver.

#### 15.3.5.1 Observability proof obligation: NULL to DATA

To verify observability, a check must be performed on each C/L gate. For each gate  $g^1, \dots, g^m$ , assertion of that gate is first computed, denoted as  $f_1, \dots, f_m = 1$ , respectively. During the NULL to DATA observability verification of  $g^n$ , where  $1 \leq n \leq m$ , the output of  $g^n$  is forced to 0. Simulation of a circuit with  $g^n$  forced to 0 is called a Gn0 simulation, and the resulting function is  $nclcktGn0(i^1, \dots, i^p)$ . To formulate the DATA to NULL observability proof obligation, the circuit must first be symbolically initialized with all possible threshold gate outputs that assert  $g^n$  after a transition from NULL to DATA. This is done by first initializing the circuit to the NULL state (i.e., all threshold gates are set to 0) and then stepping the circuit with valid symbolic DATA (i.e., not NULL and not illegal) inputs, identified as *step A*. The symbolic values of the threshold gates from *step A* are retained as  $g_B^1, \dots, g_B^m$ , and the circuit is symbolically stepped again with new inputs, identified as *step B*, which represents the DATA to NULL transition. During the verification of  $g^n$ , where  $1 \leq n \leq m$ , the output of  $g^n$  is forced to 1. Simulation of a circuit with  $g^n$  forced to 1 is called a Gn1 simulation, and the resulting function is  $nclcktGn1(i^1, \dots, i^p)$ . Additional predicates used in the proof obligations for observability are given in Table 15.4.

$p_1$  states that all the threshold gates' current output value is 0, which indicates that the circuit is in the NULL state before a DATA transition.  $p_4$  indicates that every circuit input is valid DATA.  $p_9$  assigns the outputs of the NCL circuit for a Gn0 simulation, where the output of  $g^n$ , the gate under test, is forced to 0.  $p_{10}$  enables only valid input combinations that would assert  $g^n$  to be used to step the circuit in  $p_9$ . Finally,  $p_{11}$  ensures that at least one of the outputs is NULL. The proof obligation to test observability of the NULL to DATA transition is given below as *PO5*, which tests observability of all gates,  $g^1, \dots, g^m$ . If true for  $g^n$ , this ensures that there is at least one output that will not be asserted if  $g^n$  is not asserted, for all

Table 15.4 Additional proof obligation predicates for observability

$p_n$	Predicate
$p_9$	$(o_A^1, \dots, o_A^q) = nclcktGn0(i_A^1, \dots, i_A^p)$
$p_{10}$	$f_n = 1$
$p_{11}$	$\bigvee_{n=1}^{n=q} (o_B^n = 0b00)$
$p_{12}$	$\bigwedge_{n=1}^{n=p} (i_B^n = 0b00)$
$p_{13}$	$(o_B^1, \dots, o_B^q) = nclcktGn1(i_B^1, \dots, i_B^p)$
$p_{14}$	$\sim \bigwedge_{n=1}^{n=q} (o_B^n = 0b00)$

sets of inputs in which  $g^n$  should be asserted, therefore proving that  $g^n$  is observable for the NULL to DATA transition.

$$PO5 : \bigwedge_{n=1}^{n=m} (\{p_1 \wedge p_4 \wedge p_9 \wedge p_{10}\} \rightarrow p_{11})$$

### 15.3.5.2 Observability proof obligation: DATA to NULL

Like input-completeness, NCL circuits consisting only of NCL gates with hysteresis are inherently observable for the DATA to NULL transition if observable for the NULL to DATA transition, since gate hysteresis ensures that a gate output cannot transition to 0 until all its preceding gates' outputs transition to 0. However, this is not the case for relaxed NCL circuits, which are comprised of both threshold gates with hysteresis and Boolean gates. Hence, for relaxed NCL circuits, observability of the DATA to NULL transition must also be checked.

$p_1$  initializes all threshold gate outputs to 0 before *step A*.  $p_4$  indicates that all *step A* inputs are DATA.  $p_5$  represents the symbolic step of the circuit with all threshold gates set to 0 and all inputs set to DATA, with the new values of the threshold gates stored in  $(g_B^1, \dots, g_B^m)$ .  $p_{10}$  enables only valid input combinations that would assert  $g^n$  to be used to step the circuit in  $p_5$ .  $p_{12}$  indicates that all inputs for *step B* have transitioned to NULL.  $p_{13}$  assigns the outputs of the NCL circuit for a Gn1 simulation, where the output of  $g^n$ , the gate under test, is forced to 1. Finally,  $p_{14}$  ensures that all outputs are not NULL. The proof obligation to test observability of the DATA to NULL transition is given below as *PO6*, which tests observability of all gates,  $g^1, \dots, g^m$ . If true for  $g^n$ , this ensures that following a NULL to DATA transition that asserts  $g^n$ , there is at least one output that will not become NULL during the subsequent DATA to NULL transition while  $g^n$  remains asserted, therefore proving that  $g^n$  is observable for the DATA to NULL transition.

$$PO6 : \bigwedge_{n=1}^{n=m} (\{p_1 \wedge p_4 \wedge p_5 \wedge p_{10} \wedge p_{12} \wedge p_{13}\} \rightarrow p_{14})$$

Table 15.5 Observability verification times (s)

Circuit	N to D	D to N
<i>umult4</i>	0.001	0.001
<i>umult5</i>	8.203	8.944
<i>umult6</i>	13.7599	16.1921
<i>umult7</i>	27.8229	36.528
<i>umult8</i>	54.062	105.4979
<i>umult9</i>	138.3139	412.605
<i>umult10</i>	363.7079	1,968.434
<i>umult11</i>	902.046	9,657.475
<i>umult12</i>	2,384.504	52,093.64
<i>umult13</i>	5,797.037	<b>TO</b>
<i>C432M1</i>	1.53	3.882

### 15.3.5.3 Observability results

Verification of the proof obligations for observability can be performed using any SMT solver. To perform observability verification, we developed a tool to automatically generate the circuit model and proof obligation specifications, encoded in SMT-LIB format, from the original circuit netlist, such as the one shown in Figure 15.2(a) for the  $3 \times 3$  multiplier. For the verification results presented here,  $N$ -bit  $\times$   $N$ -bit unsigned dual-rail NCL multipliers were used as benchmarks, where  $3 \leq N \leq 13$ . The ISCAS-85 C432 27-channel interrupt controller circuit was also used as a benchmark [18]. The verification proof obligations were checked using the Z3 SMT solver on an Intel<sup>®</sup> Core<sup>™</sup> i7-4790 CPU with 32GB of RAM, running at 3.60 GHz.

The verification results are listed in Table 15.5, where the first column is the Circuit name, the second column is the verification time for the NULL to DATA proof obligation, and the third column is the verification time for the DATA to NULL proof obligation. *umultN* represents an  $N$ -bit  $\times$   $N$ -bit unsigned multiplier constructed using only NCL gates with hysteresis, while *r-umultN* represents a relaxed version of the  $N$ -bit  $\times$   $N$ -bit multiplier, where NCL gates are replaced with Boolean gates when hysteresis is not required. TO is listed in the verification results when the verification time exceeded 1 day.

The test multipliers were designed exactly the same as the ones used for testing input-completeness (i.e., input-complete AND functions generate the  $X_i Y_i$  partial products, and input-incomplete AND functions generate the  $X_i Y_j$  partial products, where  $i \neq j$ ). To create buggy multipliers that were input-complete but not observable, an HA was chosen at random and the XOR function to generate its sum (i.e., the two TH24comp gates in Figure 15.1(d)) was replaced with the unobservable XOR function, shown in Figure 15.5. To check observability of relaxed circuits, the M1 module of the ISCAS-85 C432 benchmark [21] was used, where the nine-input NAND function that generates  $PA$  was composed of two relaxed input-incomplete four-input AND functions, followed by an

AQ10

 


Figure 15.5 Unobservable NCL XOR

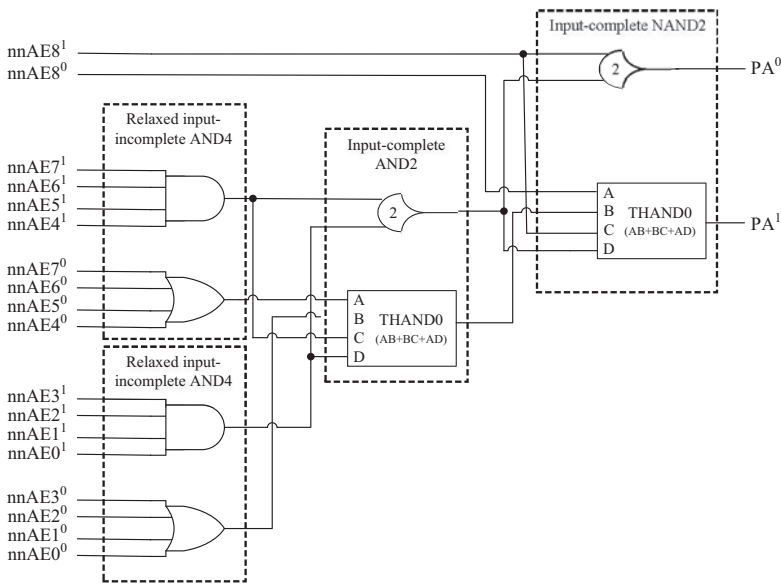


Figure 15.6 ISCAS-85 C432 M1 module nine-input NCL NAND that generates PA

input-complete two-input AND function, and then an input-complete two-input NAND function, as shown in Figure 15.6. To create a buggy version that was input-complete but not observable, either of the two gates comprising the two-input AND function in Figure 15.6 could be relaxed. The test times reported for the circuits are for testing every single gate for observability, even if a previous gate was found to be unobservable. Therefore, the time to detect a buggy circuit will be less than or equal to the reported times, since the rest of the gates would no longer need to be tested once an unobservable gate was identified. Z3 reported all bugs along with a counter example.

### 15.4 Equivalence verification for sequential NCL circuits

As described in Section 15.3.1, our equivalence verification methodology proved to be a fast and scalable approach for C/L NCL circuits. Hence, in this section we extend that approach to verify both safety and liveness of sequential NCL circuits, which is more complex due to datapath feedback.

To describe our methodology, we'll use an unsigned Multiply and Accumulate (MAC) unit as an example circuit. Figure 15.7(a) shows a synchronous MAC, where  $A' = A + X \times Y$ ; and Figure 15.7(b) shows the equivalent NCL version. The four-phase QDI handshaking protocol utilized for NCL circuits requires at least  $2N + 1$  NCL registers in a feedback loop that contains  $N$  DATA tokens, in order to avoid deadlock [12].

Hence, at least three NCL registers are needed in the MAC feedback loop to avoid deadlock, as shown in Figure 15.7(b). Although the synchronous and NCL MACs seem similar, they are structurally very different. Synchronous registers are clocked, whereas alternating DATA/NULL transitions in NCL are maintained via C-elements and a well-defined handshaking scheme.  $K_i$  and  $K_o$  are the external request input and *acknowledge* output, respectively.

Figure 15.8 shows the datapath diagram for a  $4 + 2 \times 2$  NCL MAC with two C/L stages and four registers in the feedback loop (note that including a 4th register

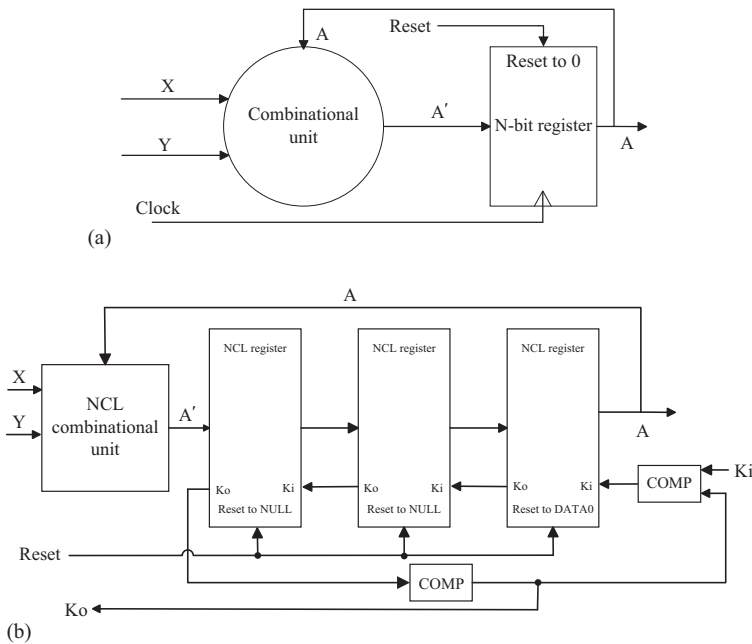


Figure 15.7 MAC circuit: (a) synchronous; (b) NCL

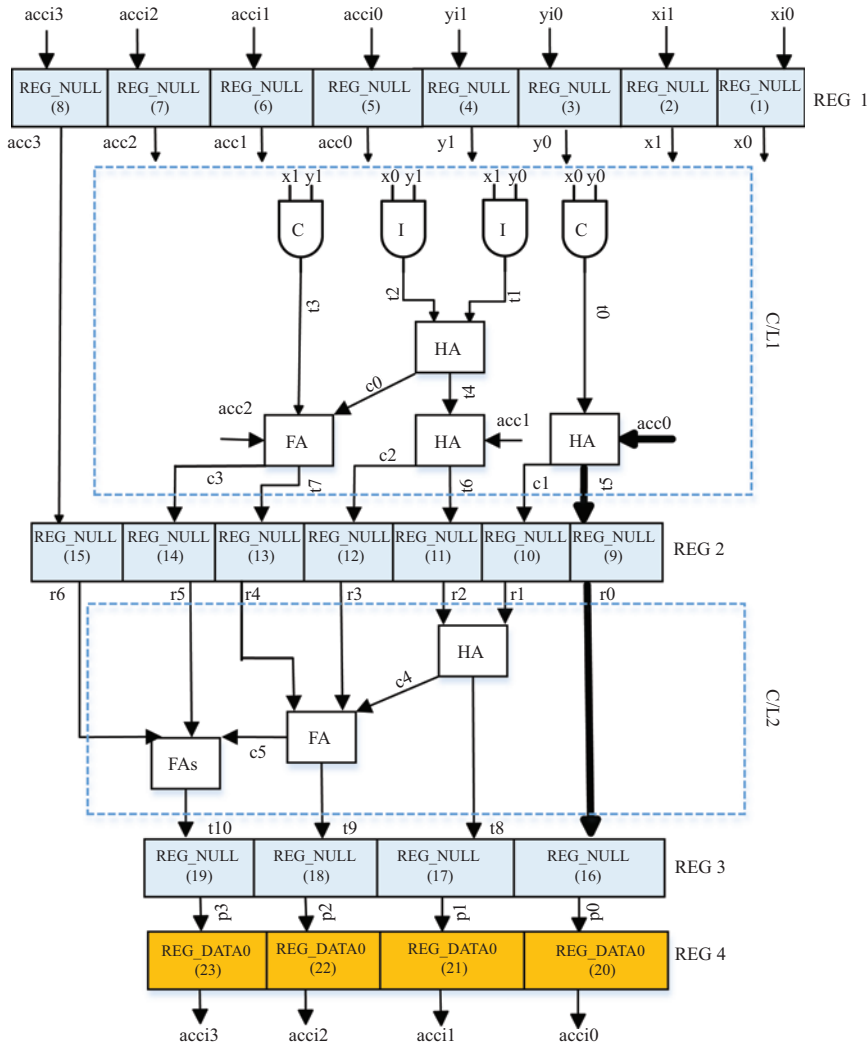


Figure 15.8  $4 + 2 \times 2$  NCL MAC datapath

in the feedback loop increases throughput compared to using the minimum required three registers, since this allows the DATA and NULL wavefronts to flow more independently [12]).  $(X_i, X_0)$  and  $(Y_i, Y_0)$  are the two bits of inputs  $X_i$  and  $Y_i$ , respectively. The product of  $X_i$  and  $Y_i$  is added with the 4-bit accumulator output,  $Acc_i$ , where  $Acc_3$  and  $Acc_0$  are the MSB and LSB, respectively. All signals shown in Figure 15.8 are dual-rail signals. HA and FA are the NCL half-adder and full-adder components, shown in Figure 15.1(d) and (e), respectively; and FA is a full-adder component without a carry output; hence, it utilizes two two-input XOR

AQ11

functions, each comprised of two TH24comp gates (same as the HA *sum* output shown in Figure 15.1(d)), to compute its *sum* output. The highlighted components in Figure 15.8 are the NCL registers.

Figure 15.9(a) shows the netlist of the NCL  $4 + 2 \times 2$  MAC, following the same structure as described in Section 15.3.1. The first two lines are the circuit inputs and outputs, respectively; lines 3–38 are the NCL threshold gates; lines 39–61 are the NCL registers; and lines 62–69 are C-elements used in the handshaking network.

### 15.4.1 Safety

Safety verification requires two steps. In the first step, we take a sequential NCL circuit and convert it to an equivalent synchronous circuit. We utilize the theory of WEB refinement [2] to compare the synchronous netlist generated from the NCL circuit with the original synchronous specification, as the notion of correctness. The major advantage of applying WEB refinement to the generated equivalent synchronous circuit instead of the actual NCL circuit is that a synchronous circuit is much more deterministic compared to its NCL equivalent, which makes the verification time much faster. The generated synchronous circuit, specification synchronous circuit, and the WEB-refinement property are automatically encoded in the SMT-LIB language. The resulting equivalence property is then checked using an SMT solver. In the second step, we check the invariant for each C/L stage, the same as previously discussed in Section 15.3.2.

The converted netlist (NCL-SYNC) is depicted in Figure 15.9(b). The conversion algorithm for sequential NCL circuits is slightly different than for C/L NCL circuits, described in Section 15.3.1, since the sequential NCL circuit contains reset-to-DATA registers, which are replaced with a 2-bit resettable synchronous register, 1 bit for each rail of the corresponding NCL dual-rail register. Like for C/L NCL circuits, all reset-to-NUL registers, handshaking signals, and C-elements are eliminated; and all C/L NCL gates are replaced with their corresponding relaxed (i.e., Boolean) gate.

The NCL-SYNC netlist must next be checked against the synchronous specification (SPEC-SYNC) netlist for equivalence. When verifying C/L NCL circuits, the circuit functionality could be specified as a Boolean function. However, since sequential circuits involve states and transitions, we use TSs as the formal model to capture the behaviors of both the NCL-SYNC netlist as well as the SPEC-SYNC netlist. The theory of WEB refinement [2] defines what it means for an implementation TS to be functionally equivalent to a specification TS. Therefore, we use the theory of WEB refinement for checking equivalence for sequential circuits.

The theory of WEB refinement allows for stutter between the implementation TS and the specification TS. What this means is that multiple but finite transitions of the implementation can match to a single specification transition. Rank functions (functions that map circuit states to natural numbers) are used to distinguish finite stutter from deadlock (infinite stutter). Another characteristic of WEB refinement is the use of refinement maps, which are functions that map implementation states to

<pre> 1. xi0_0,xi0_1,xi1_0,xi1_1,yi0_0,yi0_1,yi1_0,yi1_1 2. acci0_0,acci0_1,acci1_0,acci1_1,...,acci3_0,acci3_1 3. th22 x0_1,y0_1 t0_1 4. thand0 y0_0,x0_0,y0_1,x0_1 t0_0 5. th12 x1_0,y0_0 t1_0 6. th22 x1_1,y0_1 t1_1 7. th12 x0_0,y1_0 t2_0 8. th22 x0_1,y1_1 t2_1 9. th12 x1_0,y1_0 t3_0 10. th22 x1_1,y1_1 t3_1 11. th24comp t2_0,t1_1,t1_0,t2_1 t4_0 12. th24comp t2_0,t1_0,t2_1,t1_1 t4_1 13. th12 t2_0,t1_0 c0_0 14. th22 t1_1,t2_1 c0_1 15. th24comp acc0_0,t0_1,t0_0,acc0_1 t5_0 16. th24comp acc0_0,t0_0,acc0_1,t0_1 t5_1 17. th12 acc0_0,t0_0 c1_0 18. th22 t0_1,acc0_1 c1_1 19. th24comp acc1_0,t4_1,t4_0,acc1_1 t6_0 20. th24comp acc1_0,t4_0,acc1_1,t4_1 t6_1 21. th12 acc1_0,t4_0 c2_0 22. th22 t4_1,acc1_1 c2_1 23. th23 t3_0,acc2_0,c0_0 c3_0 24. th23 t3_1,acc2_1,c0_1 c3_1 25. th34w2 c3_1,t3_0,acc2_0,c0_0 t7_0 26. th34w2 c3_0,t3_1,acc2_1,c0_1 t7_1 27. th24comp r1_0,r2_1,r2_0,r1_1 t8_0 28. th24comp r1_0,r2_0,r1_1,r2_1 t8_1 29. th12 r1_0,r2_0 c4_0 30. th22 r2_1,r1_1 c4_1 31. th23 r4_0,r3_0,c4_0 c5_0 32. th23 r4_1,r3_1,c4_1 c5_1 33. th34w2 c5_1,r4_0,r3_0,c4_0 t9_0 34. th34w2 c5_0,r4_1,r3_1,c4_1 t9_1 35. th24comp r5_0,r6_1,r6_0,r5_1 c6_0 36. th24comp r5_0,r6_0,r5_1,r6_1 c6_1 37. th24comp c5_0,c6_1,c6_0,c5_1 t10_0 38. th24comp c5_0,c6_0,c5_1,c6_1 t10_1 39. Reg_NULL 1 xi0_0,xi0_1 KO2 ko1 x0_0,x0_1 40. Reg_NULL 1 xi1_0,xi1_1 KO2 ko2 x1_0,x1_1 41. Reg_NULL 1 yi0_0,yi0_1 KO2 ko3 y0_0,y0_1 42. Reg_NULL 1 yi1_0,yi1_1 KO2 ko4 y1_0,y1_1 43. Reg_NULL 1 acci0_0,acci0_1 KO2 ko5 acc0_0,acc0_1 44. Reg_NULL 1 acci1_0,acci1_1 KO2 ko6 acc1_0,acc1_1 45. Reg_NULL 1 acci2_0,acci2_1 KO2 ko7 acc2_0,acc2_1 46. Reg_NULL 1 acci3_0,acci3_1 KO2 ko8 acc3_0,acc3_1 47. Reg_NULL 2 t5_0,t5_1 ko16 ko9 r0_0,r0_1 48. Reg_NULL 2 c1_0,c1_1 KO3 ko10 r1_0,r1_1 49. Reg_NULL 2 t6_0,t6_1 KO3 ko11 r2_0,r2_1 50. Reg_NULL 2 c2_0,c2_1 KO3 ko12 r3_0,r3_1 51. Reg_NULL 2 t7_0,t7_1 KO3 ko13 r4_0,r4_1 52. Reg_NULL 2 c3_0,c3_1 KO3 ko14 r5_0,r5_1 53. Reg_NULL 2 acc3_0,acc3_1 KO3 ko15 r6_0,r6_1 54. Reg_NULL 3 r0_0,r0_1 ko20 ko16 p0_0,p0_1 55. Reg_NULL 3 t8_0,t8_1 ko21 ko17 p1_0,p1_1 56. Reg_NULL 3 t9_0,t9_1 ko22 ko18 p2_0,p2_1 57. Reg_NULL 3 t10_0,t10_1 ko23 ko19 p3_0,p3_1 58. Reg_DATA0 4 p0_0,p0_1 KO4 ko20 acci0_0,acci0_1 59. Reg_DATA0 4 p1_0,p1_1 KO5 ko21 acci1_0,acci1_1 60. Reg_DATA0 4 p2_0,p2_1 KO6 ko22 acci2_0,acci2_1 61. Reg_DATA0 4 p3_0,p3_1 KO7 ko23 acci3_0,acci3_1 62. C4 ko9,ko10,ko11,ko12 KO1 63. C4 ko13,ko14,ko15,KO1 KO2 64. C3 ko17,ko18,ko19 KO3 65. C2 Ki,ko5 KO4 66. C2 Ki,ko6 KO5 67. C2 Ki,ko7 KO6 68. C2 Ki,ko8 KO7 69. C4 ko1,ko2,ko3,ko4 KO </pre>	<pre> 1. xi0_1,xi1_1,yi0_1,yi1_1 2. acci0_0,acci0_1,acci1_0,acci1_1,...,acci3_0,acci3_1 3. not xi0_1 xi0_0 4. not yi0_1 yi0_0 5. not xi1_1 xi1_0 6. not yi1_1 yi1_0 7. th12 xi0_0,yi0_0 t0_0 8. th22 xi0_1,yi0_1 t0_1 9. th12 xi1_0,yi0_0 t1_0 10. th22 xi1_1,yi0_1 t1_1 11. th12 xi0_0,yi1_0 t2_0 12. th22 xi0_1,yi1_0 t2_1 13. th12 x1_0,y1_0 t3_0 14. th22 x1_1,y1_1 t3_1 15. th24comp t2_0,t1_1,t1_0,t2_1 t4_0 16. th24comp t2_0,t1_0,t2_1,t1_1 t4_1 17. th12 t2_0,t1_0 c0_0 18. th22 t1_1,t2_1 c0_1 19. th24comp acci0_0,t0_1,t0_0,acci0_1 t5_0 20. th24comp acci0_0,t0_0,acci0_1,t0_1 t5_1 21. th12 acci0_0,t0_0 c1_0 22. th22 t0_1,acci0_1 c1_1 23. th24comp acci1_0,t4_1,t4_0,acci1_1 t6_0 24. th24comp acci1_0,t4_0,acci1_1,t4_1 t6_1 25. th12 acci1_0,t4_0 c2_0 26. th22 t4_1,acci1_1 c2_1 27. th23 t3_0,acci2_0,c0_0 c3_0 28. th23 t3_1,acci2_1,c0_1 c3_1 29. th34w2 c3_1,t3_0,acci2_0,c0_0 t7_0 30. th34w2 c3_0,t3_1,acci2_1,c0_1 t7_1 31. th24comp c1_0,t6_1,t6_0,c1_1 t8_0 32. th24comp c1_0,t6_0,c1_1,t6_1 t8_1 33. th12 c1_0,t6_0 c4_0 34. th22 t6_1,c1_1 c4_1 35. th23 t7_0,c2_0,c4_0 c5_0 36. th23 t7_1,c2_1,c4_1 c5_1 37. th34w2 c5_1,t7_0,c2_0,c4_0 t9_0 38. th34w2 c5_0,t7_1,c2_1,c4_1 t9_1 39. th24comp c3_0,acci3_1,acci3_0,c3_1 c6_0 40. th24comp c3_0,acci3_0,c3_1,acci3_1 c6_1 41. th24comp c5_0,c6_1,c6_0,c5_1 t10_0 42. th24comp c5_0,c6_0,c5_1,c6_1 t10_1 43. Reg_0 t5_0,t5_1 acci0_0,acci0_1 44. Reg_0 t8_0,t8_1 acci1_0,acci1_1 45. Reg_0 t9_0,t9_1 acci2_0,acci2_1 46. Reg_0 t10_0,t10_1 acci3_0,acci3_1 </pre>
(a)	(b)

Figure 15.9 (a)  $4 + 2 \times 2$  NCL MAC netlist. (b) Converted synchronous equivalent netlist



specification states. Refinement maps allow for the implementation and specification to be specified at significantly different abstraction levels. However, since the rail<sup>1</sup> registers of NCL-SYNC and the registers of SPEC-SYNC have a one-to-one mapping, there is no stutter between these two TSs, and the refinement is simply a projection of the rail<sup>1</sup> registers of the implementation state to the registers of the specification state. Therefore, the correctness proof obligations required for verifying WEB refinement can be reduced to the proof obligation depicted in Figure 15.10, where  $s$  is a state of NCL-SYNC;  $u$  is a SPEC-SYNC state obtained by projecting the values of the rail<sup>1</sup> registers from state  $s$ ;  $Step_{SYNC\_NCL}$  and  $Step_{SYNC\_SPEC}$  are the functions that correspond to a single step of the NCL-SYNC circuit and the SPEC-SYNC circuit, respectively;  $w$  is the state obtained by stepping NCL-SYNC from state  $s$ ; and  $v$  is the state obtained by stepping SPEC-SYNC from state  $u$ . The proof obligation states that the two circuits are functionally equivalent if for every state  $s$  of NCL-SYNC, the corresponding projection of values from the rail<sup>1</sup> registers of the  $w$  state are equivalent to the values of the corresponding registers in the  $v$  state. This proof obligation can be encoded in the SMT-LIB language, as shown below in *PO7*, and checked using an SMT solver.

$$\begin{aligned}
 PO7: \{ \forall s :: s \in S_{SYNC\_NCL} :: \\
 & [u = Reg\_Proj(s) \wedge w = Step_{SYNC\_NCL}(s) \wedge v = Step_{SYNC\_SPEC}(u)] \\
 & \Rightarrow Reg\_Proj(w) = v \}.
 \end{aligned}$$

After verifying function equivalence, the rail<sup>0</sup> outputs of each C/L stage must also be checked to ensure safety, as detailed in Section 15.3.2. Note that for sequential circuits, which include datapath feedback, the first invariant check method that checks the entire circuit simultaneously won't work; hence, the second, much faster method that performs the invariant check independently for each stage is utilized.

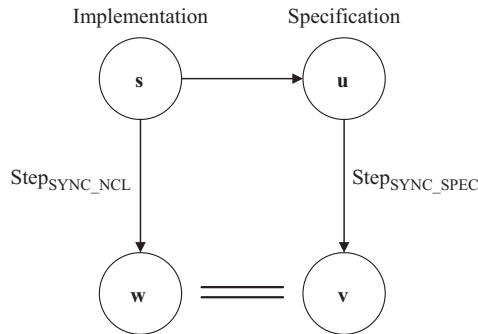


Figure 15.10 Depiction of proof obligation to check equivalence of NCL-SYNC and SPEC-SYNC netlists

15.4.2 Liveness

Figure 15.11 shows the handshaking connections for the  $4 + 2 \times 2$  NCL MAC. Full-word completion is used by the input register, Reg 1, to generate a single  $Ko$ . Full-word completion is also utilized between Reg 1 and Reg 2, since bit-wise completion would have the same delay and require more area. Partial bit-wise

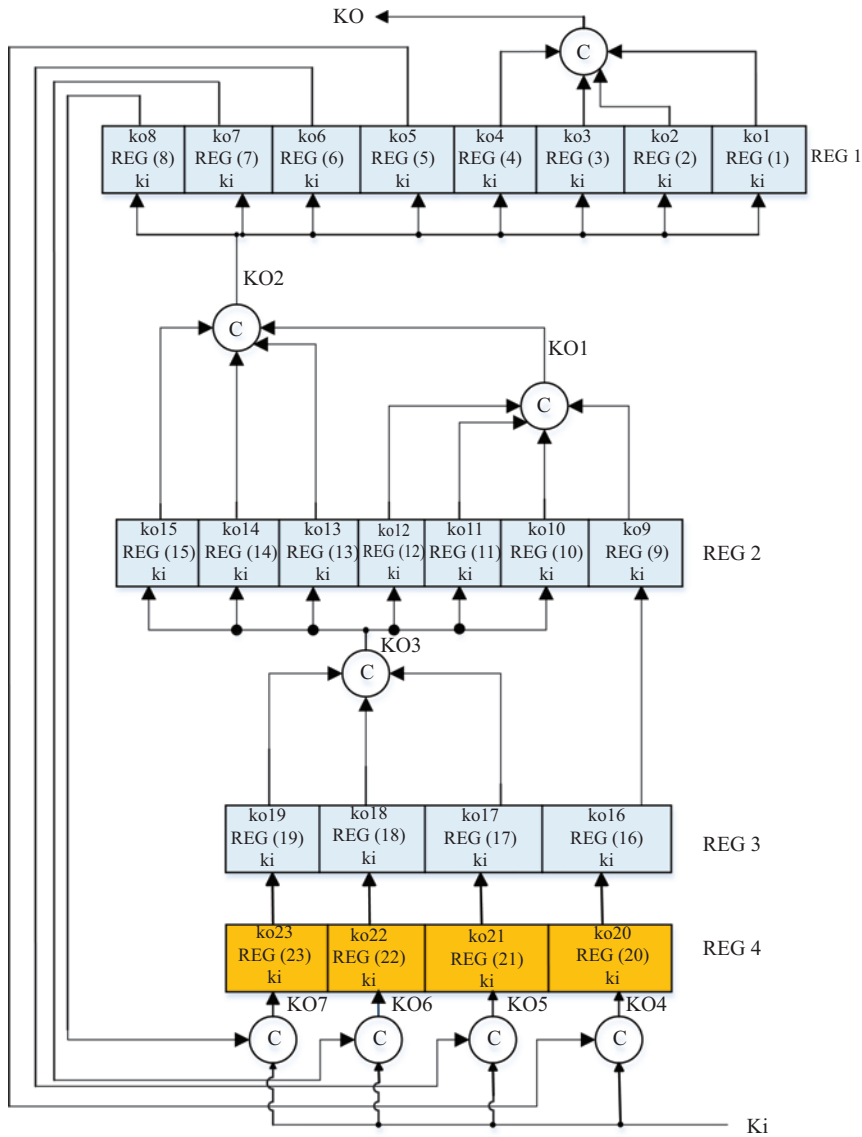


Figure 15.11 Handshaking connections for the  $4 + 2 \times 2$  NCL MAC

completion is utilized between Reg 2 and Reg 3, since full bit-wise completion would have the same delay and require more area. Bit-wise completion is utilized between Reg 3 and Reg 4, and for the output register, Reg 4. The handshaking check for sequential NCL circuits is essentially the same as that for C/L NCL circuits, described in Section 15.3.3. The only addition is calculating a feedback register's level, which should be assigned the same level as other registers that share its  $K_i$  input signal, or one level more than its previous register, if its  $K_i$  input signal is not shared with another register already assigned a level. For the MAC example in Figure 15.11, feedback registers 5–8 would be assigned level 1, since they share their  $K_i$  input with the other level 1 registers, 1–4; and feedback register 15 would be assigned level 2, since it shares its  $K_i$  input with other level 2 registers, 9–14. Figure 15.12 shows the *reg\_fanin* and *ko\_fanout* lists for each register in the  $4 + 2 \times 2$  NCL MAC example.

After verifying handshaking correctness, each stage's C/L must also be checked for input-completeness and observability, utilizing the methods detailed in Sections 15.3.4 and 15.3.5, respectively, to guarantee liveness.

1: reg_fanin: 0	ko_fanout: 0
2: reg_fanin: 0	ko_fanout: 0
3: reg_fanin: 0	ko_fanout: 0
4: reg_fanin: 0	ko_fanout: 0
5: reg_fanin: [20]	ko_fanout: [20]
6: reg_fanin: [21]	ko_fanout: [21]
7: reg_fanin: [22]	ko_fanout: [22]
8: reg_fanin: [23]	ko_fanout: [23]
9: reg_fanin: [1, 3, 5]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
10: reg_fanin: [1, 3, 5]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
11: reg_fanin: [1, 2, 3, 4, 6]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
12: reg_fanin: [1, 2, 3, 4, 6]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
13: reg_fanin: [1, 2, 3, 4, 7]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
14: reg_fanin: [1, 2, 3, 4, 7]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
15: reg_fanin: [8]	ko_fanout: [1, 2, 3, 4, 5, 6, 7, 8]
16: reg_fanin: [9]	ko_fanout: [9]
17: reg_fanin: [10, 11]	ko_fanout: [10, 11, 12, 13, 14, 15]
18: reg_fanin: [10, 11, 12, 13]	ko_fanout: [10, 11, 12, 13, 14, 15]
19: reg_fanin: [10, 11, 12, 13, 14, 15]	ko_fanout: [10, 11, 12, 13, 14, 15]
20: reg_fanin: [16]	ko_fanout: [16]
21: reg_fanin: [17]	ko_fanout: [17]
22: reg_fanin: [18]	ko_fanout: [18]
23: reg_fanin: [19]	ko_fanout: [19]

Figure 15.12 *reg\_fanin* and *ko\_fanout* lists for the  $4 + 2 \times 2$  NCL MAC

Table 15.6 *Verification results for sequential NCL circuits*

Circuits	Functional check (s)	Handshaking check (s)	Total time (s)
ISCAS s27	0.01	0.0019	0.0119
4 + 2 × 2 MAC	0.01	0.0045	0.0145
8 + 4 × 4 MAC	0.05	0.7852	0.8352
12 + 6 × 6 MAC	0.77	2.331	3.101
16 + 8 × 8 MAC	47.55	21.7411	69.2911
20 + 10 × 10 MAC	2,643.99	163.6463	2,807.6363
20 + 10 × 10 MAC-B1	0.11 (B)	163.6463	163.7563
20 + 10 × 10 MAC-B2	0.13 (B)	163.6463	163.7763
20 + 10 × 10 MAC-B3	2,643.99	169.8422 (B)	2,813.8322
20 + 10 × 10 MAC-B4	2,643.99	159.3253 (B)	2,803.3153
20 + 10 × 10 MAC-B5	0.20 (B)	163.6463	163.8463

### 15.4.3 *Sequential NCL circuit results*

The verification results for sequential NCL circuits, including functional equivalence and handshaking checks, are shown in Table 15.6. Since the invariant, input-completeness, and observability checks are exactly the same for combinational and sequential NCL circuits, these results are not included in Table 15.6. Test circuits include multiple MAC units and one ISCAS-89 benchmark, s27 [22]. The MAC units are represented as  $A + M \times N$ , where  $A$ ,  $M$ , and  $N$  represent the length of the accumulator, multiplicand, and multiplier, respectively. The same types of bugs were tested for the MACs as tested for the multipliers, and the same machine was used to perform the sequential circuit verification, both as described at the end of Section 15.3.3. Z3 reported all functional bugs along with a counter example, and our handshaking check tool identified and reported the location of all inserted completion logic bugs.

## 15.5 **Conclusions and future work**

This chapter presents a novel methodology for formally verifying the correctness (both safety and liveness) of combinational and sequential NCL circuits. The approach includes methods for ensuring handshaking correctness, and functional correctness of both rail<sup>1</sup> and rail<sup>0</sup> outputs, and methods to ensure that NCL C/L circuits, or pipeline stages, are both input-complete and observable, which is required for correct operation under all timing scenarios. The presented methodology is applicable to both NCL circuits designed using only NCL gates with hysteresis and relaxed NCL circuits, where NCL gates with hysteresis are replaced with their Boolean equivalent gate when hysteresis is not required for input-completeness and/or observability.

The framework of this verification methodology can also be applied to other QDI paradigms, such as MTNCL and PCHB. For MTNCL, the functional checking

AQ12

AQ13

and invariant checking methods are essentially the same as for NCL, but the handshaking check is slightly different [23]. Additionally, MTNCL circuits do not require input-completeness or observability, so these checks are not needed. For PCHB, the handshaking check is essentially the same as for NCL, but the functional checking method is a bit different [11]. Since PCHB gates consist of dual-rail input(s) and output(s), invariant, input-completeness, and observability checking are not required, as these are ensured within the primitive PCHB gates themselves.

## References

- [1] V. Wijayasekara, S.K. Srinivasan, and S.C. Smith, “Equivalence verification for NULL Convention Logic (NCL) circuits,” *32nd IEEE International Conference on Computer Design (ICCD)*, pp. 195–201, October 2014.
- [2] P. Manolios, “Correctness of pipelined machines,” in *FMCAD 2000*, ser. LNCS, W.A. Hunt, Jr. and S.D. Johnson, Eds., vol. 1954, Springer-Verlag, 2000, pp. 161–178. AQ14
- [3] D. Monniaux, “A survey of Satisfiability Modulo Theory” [online]. Available: <https://hal.archives-ouvertes.fr/hal-01332051/document> [Accessed: May 5, 2019].
- [4] C.W. Moon, P.R. Stephan, and R.K. Brayton, *Journal of VLSI Signal Processing* (1994) 7: 85. AQ15
- [5] C.J. Myers, *Asynchronous Circuit Design*. New York: Wiley, 2001.
- [6] A. Semenov and A. Yakovlev, “Verification of asynchronous circuits using time Petri net unfolding,” *33rd Design Automation Conference*, Las Vegas, NV, USA, 1996, pp. 59–62.
- [7] F. Verbeek and J. Schmaltz, “Verification of building blocks for asynchronous circuits,” in *ACL2*, ser. EPTCS, R. Gamboa and J. Davis, Eds., vol. 114, 2013, pp. 70–84. AQ16
- [8] A. Peeters, F. te Beest, M. de Wit, and W. Mallon, “Click elements: An implementation style for data-driven compilation,” *IEEE Symposium on Asynchronous Circuits and Systems*, 2010, pp. 3–14.
- [9] S.K. Srinivasan and R.S. Katti, “Desynchronization: design for verification,” in *FMCAD*, P. Bjesse and A. Slobodova, Eds., 2011, pp. 215–222.
- [10] A.A. Sakib, S.C. Smith, and S.K. Srinivasan, “Formal modeling and verification for pre-charge half buffer gates and circuits,” *60th IEEE International Midwest Symposium on Circuits and Systems*, Boston, MA, 2017, pp. 519–522.
- [11] A.A. Sakib, S.C. Smith, and S.K. Srinivasan, “An equivalence verification methodology for combinational asynchronous PCHB circuits,” *61st IEEE International Midwest Symposium on Circuits and Systems*, Windsor, ON, Canada, 2018, pp. 767–770.
- [12] S.C. Smith and J. Di, “Designing asynchronous circuits using NULL Convention Logic (NCL),” in *Synthesis Lectures on Digital Circuits and Systems*, Morgan & Claypool Publishers, vol. 4/1, July 2009.

- [13] C. Jeong and S.M. Nowick, "Optimization of robust asynchronous circuits by local input completeness relaxation," *Asia and South Pacific Design Automation Conference*, Jan. 2007, pp. 622–627.
- [14] A. Kondratyev, L. Neukom, O. Roig, A. Taubin, and K. Fant, "Checking delay-insensitivity:  $10^4$  gates and beyond," *8th International Symposium on Asynchronous Circuits and Systems*, April 2002, pp. 149–157.
- [15] L.M. de Moura and N. Bjørner, "Z3: An efficient SMT solver," in *TACAS*, ser. Lecture Notes in Computer Science, C.R. Ramakrishnan and J. Rehof, Eds., vol. 4963, Springer, 2008, pp. 337–340.
- [16] D. Bryan, "The ISCAS '85 benchmark circuits and netlist format" [online]. Available: <https://ddd.fit.cvut.cz/prj/Benchmarks/iscas85.pdf> [Accessed: May 5, 2019].
- [17] C.L. Seitz, "System timing," in *Introduction to VLSI Systems*, Boston, MA, USA: Addison Wesley Longman Publishing Co., Inc., 1979, pp. 218–262.
- [18] "ISCAS-85 c432 27-channel interrupt controller" [online]. Available: <http://web.eecs.umich.edu/~jhayes/iscas.restore/c432.html> [Accessed: May 5, 2019].
- [19] S.C. Smith, R.F. DeMara, J.S. Yuan, D. Ferguson, and D. Lamb, "Optimization of null convention self-timed circuits," *Integr. VLSI J.* (2004) 37(3): 135–165.
- [20] "ISCAS-85 c432 27-channel interrupt controller Module M3" [online]. Available: <http://web.eecs.umich.edu/~jhayes/iscas.restore/c432m3.html> [Accessed: May 5, 2019].
- [21] "ISCAS-85 c432 27-channel interrupt controller Module M1" [online]. Available: <http://web.eecs.umich.edu/~jhayes/iscas.restore/c432m1.html> [Accessed: May 5, 2019].
- [22] [Online] <http://www.pld.ttu.ee/~maksim/benchmarks/iscas89/bench/>, [Accessed: May 5, 2019].
- [23] M. Hossain, A.A. Sakib, S.K. Srinivasan, and S.C. Smith, "An equivalence verification methodology for asynchronous sleep convention logic circuits," *IEEE International Symposium on Circuits and Systems*, May 2019.

---

*Chapter 15*

**Formal verification of NCL circuits**

---

**Author Queries**

- AQ1: Please check the sentence “Testing-based approaches have ...” for sense and revise if needed.
- AQ2: Please spell out “FDIV”, if needed.
- AQ3: Please spell out “NCL” and “QDI” at first use, if needed.
- AQ4: Please provide the city, state code (if USA) and country names for the affiliation of the authors
- AQ5: Please spell out “PCHB” at first use, if needed.
- AQ6: Please spell out “SOP”, if needed.
- AQ7: Please confirm the steps after the sentence “The NCL equivalence verification method requires five steps ...” have been set correctly.
- AQ8: Please check in Figure 15.1, part (a) has been set correctly.
- AQ9: Please spell out “MSB” at first use, if needed.
- AQ10: Please spell out “PA” at first use, if needed.
- AQ11: Please spell out “LSB”, if needed.
- AQ12: Please approve edit to the sentence “The presented methodology is applicable ...”.
- AQ13: Please spell out “MTNCL” at first use, if needed.
- AQ14: Please provide publisher location for Refs. [2, 12, 15].
- AQ15: Please provide article title for Ref. [4]; please also check the page range.
- AQ16: Please provide publisher name and location for Refs. [7, 8, 9].